
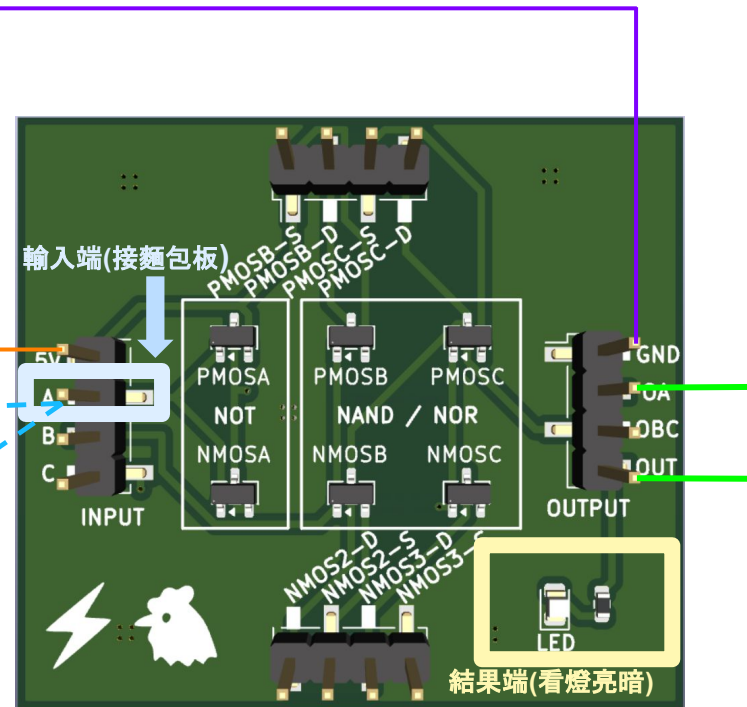
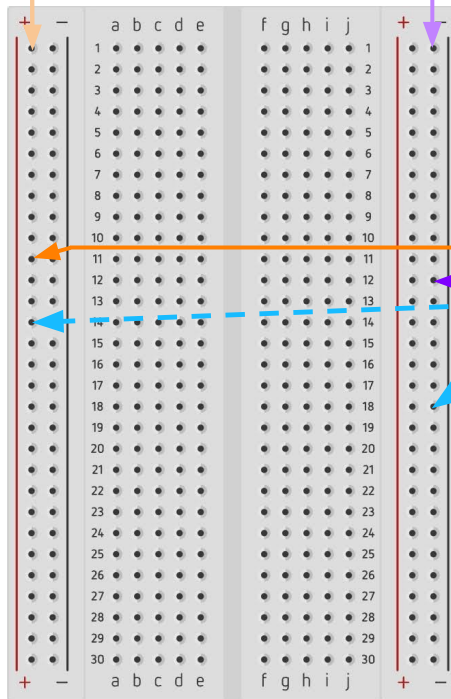





- NOT閘範例接線圖

A	OA
0	1
1	0

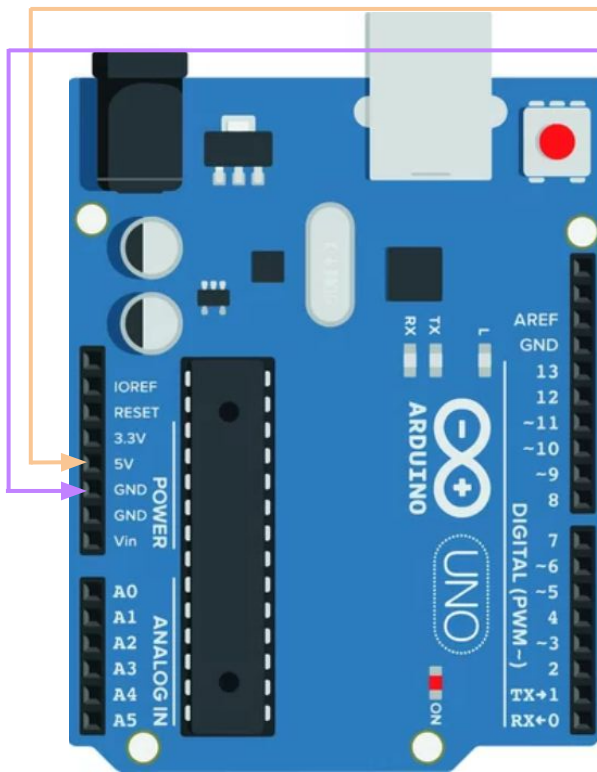


● NAND閘範例接線圖

	B	C	OBC
	0	0	1
	0	1	1
	1	0	1
	1	1	0

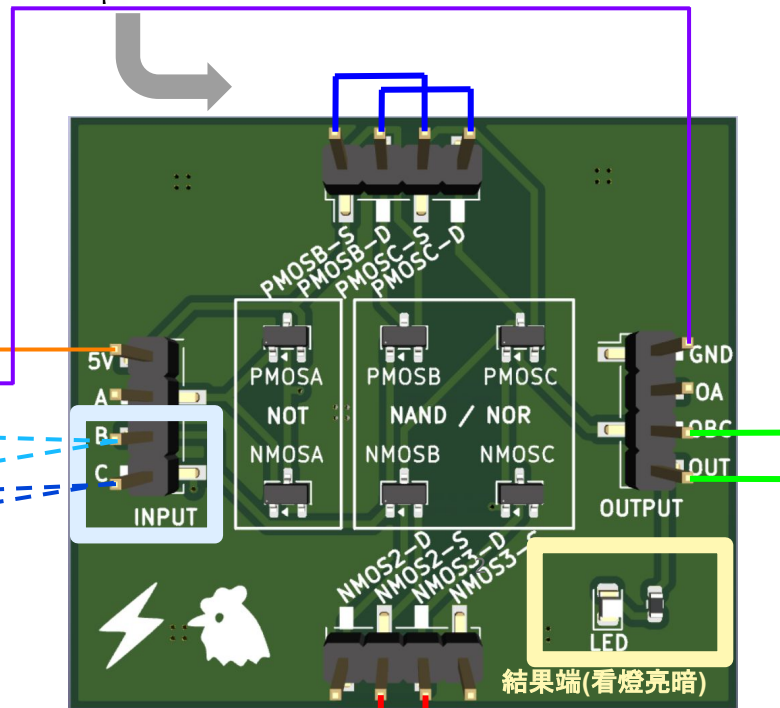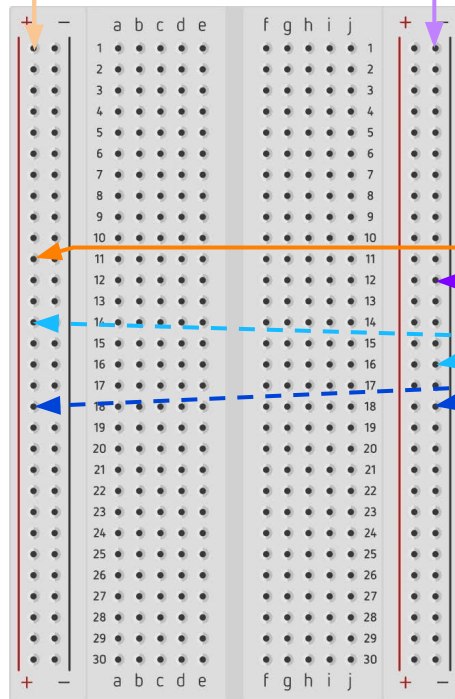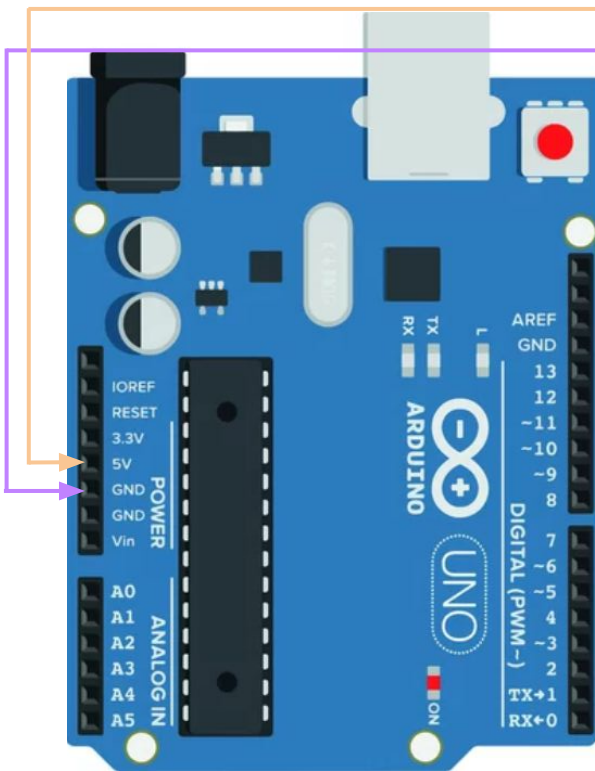


"B的S端接C的D端"(串聯)



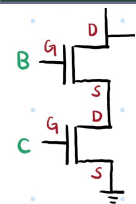


● NOR閘範例接線圖


	B	C	OBC
	0	0	1
	0	1	0
	1	0	0
	1	1	0

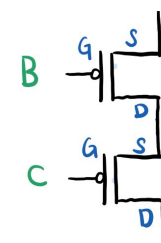

B的D端接C的S端(串聯)

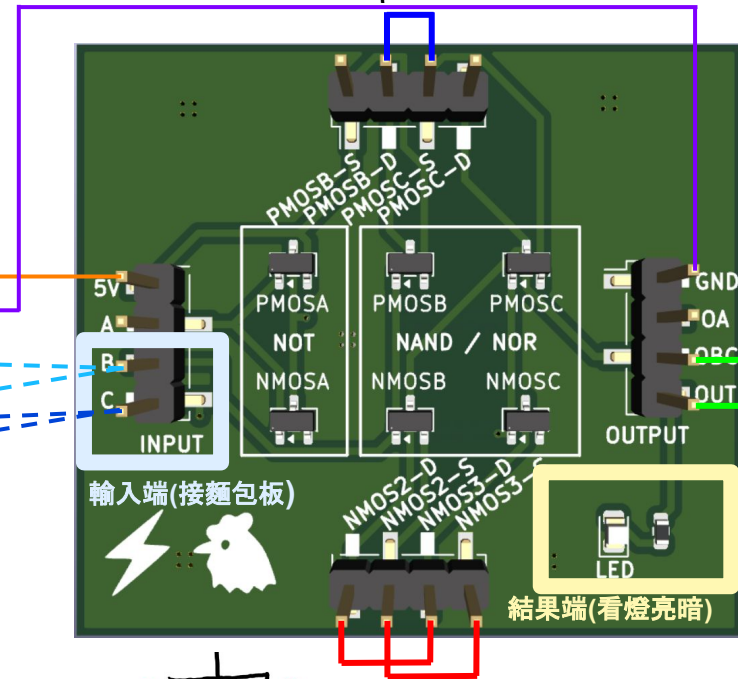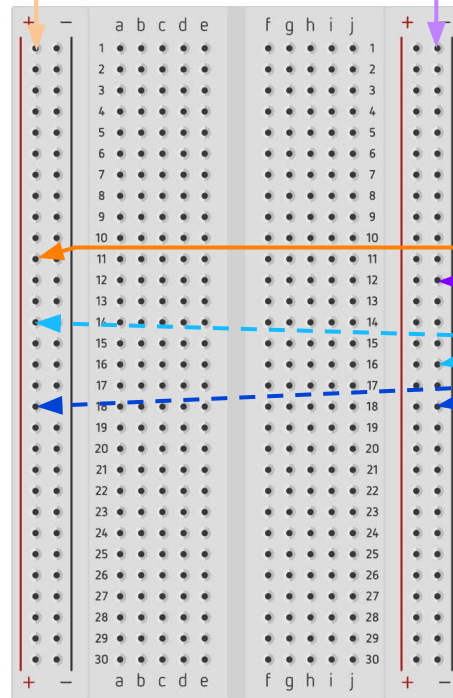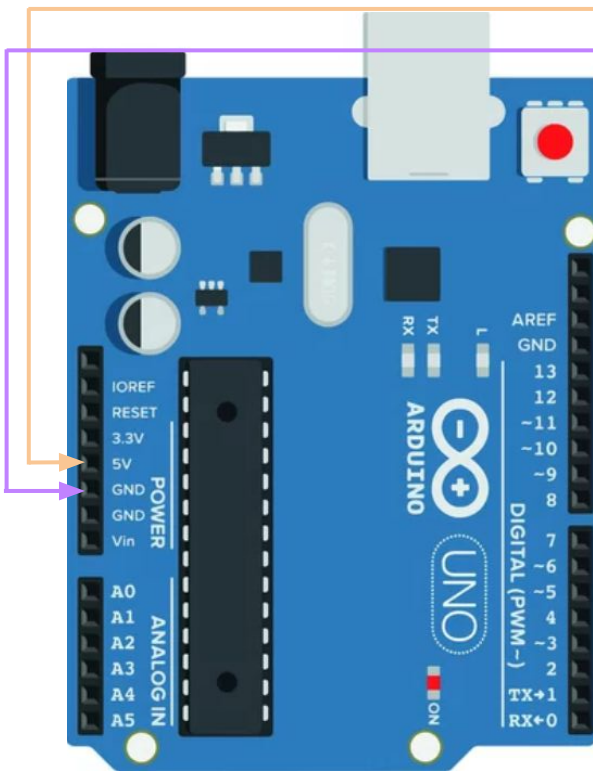


"D端對D端, S端對S端"(並聯)



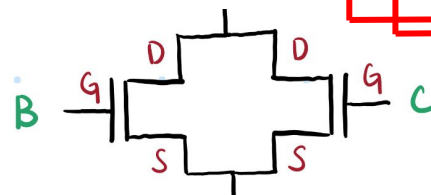


● AND閘範例接線圖

	B	C	OA
	0	0	0
	0	1	0
	1	0	0
	1	1	1

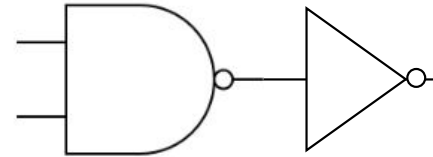


OBC接回A, 以再
執行一次反相

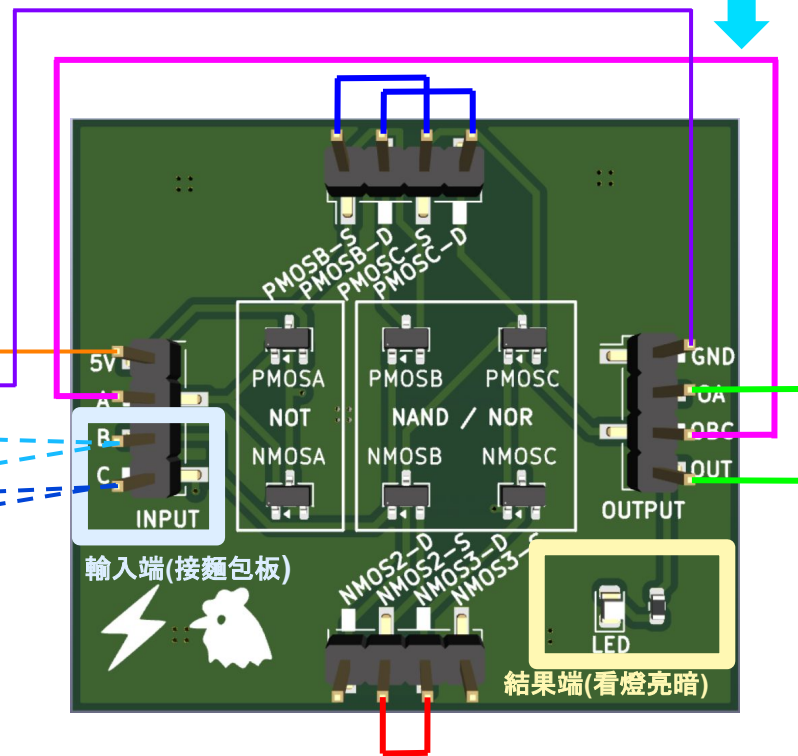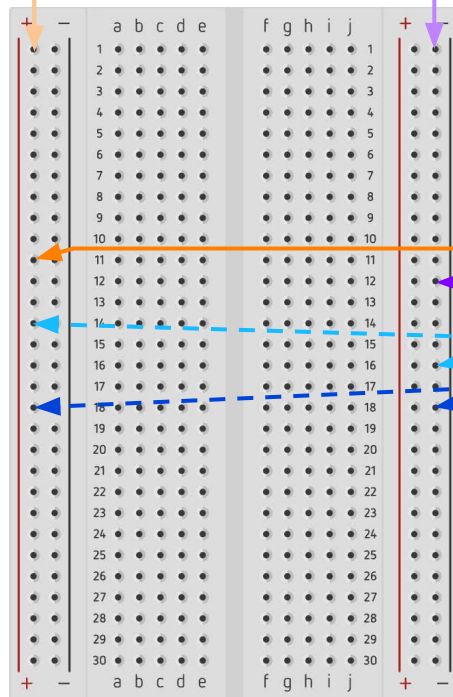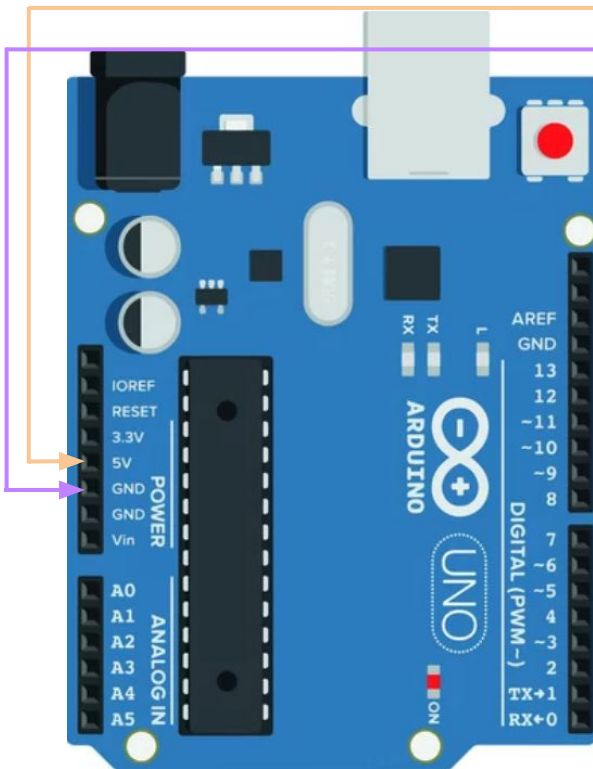

● OR閘範例接線圖

	B	C	OA
	0	0	0
	0	1	1
	1	0	1
	1	1	1

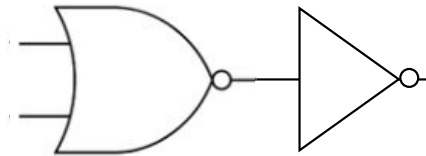

OBC接回A, 以再
執行一次反相

